

Sequential Logic Design using VHDL

Brihat Ratna Bajracharya

Department of Electronics and Computer Engineering, IOE Central Campus, Pulchowk
Lalitpur, Nepal

070bct513@ioe.edu.np

Abstract—VHDL is a language for describing digital electronic systems. VHDL is designed to fill a number of needs in the design process. Firstly, it allows description of the structure of a design, i.e. how it is decomposed into sub-designs, and how those sub-designs are interconnected. Secondly, it allows the specification of the function of designs using familiar programming language forms. Thirdly, as a result, it allows a design to be simulated before being manufactured, so that designers can quickly compare alternatives and test for correctness without the delay and expense of hardware prototyping.

I. INTRODUCTION

VHDL stands for VHSIC (Very High Speed Integrated Circuit) Hardware Descriptive Language. It is used in electronic design automation to describe digital and mixed-signal systems such as field-programmable gate arrays and integrated circuits. VHDL can also be used as a general programming language. VHDL was originally developed at the behest of the US Department of Defence in order to document the behaviour of the ASICs that supplier companies were including in equipment. VHDL is influenced from Ada and Pascal. The initial release of VHDL was designed as per IEEE 1076 standard in 1987. The most commonly used VHDL version supported by CAD tools is IEEE 1076 1993.

A. Features of VHDL

- It is a hardware descriptive language used for design entry and simulation of digital circuits.
- It is an event-driven language: i.e. whenever an event occurs on signals in VHDL, it triggers the execution of a statement.
- It allows both concurrent as well as sequential modelling.
- It gives the flexibility to define data types that are specific to user needs apart from predefined types.
- It supports code reusability and code sharing via packages and user defined libraries.
- It is case-insensitive i.e. it does not differentiate between lowercase and uppercase letters.
- It is strongly typed language i.e. it does not support implicit conversion between data types.

B. Levels of representation and abstraction

A digital system can be represented at different levels of abstraction. This keeps the description and design of complex systems manageable.

1) Behavioral – The highest level of abstraction that describes a system in terms of what it does (or how it behaves)

rather than in terms of its components and interconnection between them. A behavioural description specifies the relationship between the input and output signals. This could be a Boolean expression or a more abstract description such as the Register Transfer or Algorithmic level.

2) Structural – The structural level, on the other hand, describes a system as a collection of gates and components that are interconnected to perform a desired function. A structural description could be compared to a schematic of interconnected logic gates. It is a representation that is usually closer to the physical realization of a system.

C. Sequential Statements

The logic circuits in which the values of the output depends not only on the present values of the inputs but also on the past behaviour of the circuit are referred to as sequential circuits. A sequential circuit is described in terms of logic conditions called logic states. Sequential circuits include memory elements that store the values of the logic states. When the circuit's input changes values, the new input values either leave the circuit in the same state or cause it to change into a new state. Over time the circuit changes through a sequence of states as a result of changes in the inputs. Circuits that behave in this way are referred to as sequential circuits. The general structure of a sequential circuit is shown in figure.


 


Fig. Sequential circuit block diagram

A stable state of a sequential circuit is described as previous, present, or next. The present state is the present logic output of the circuit. The previous state is the logic output of the circuit before the present state. The next state is the logic output of the circuit after the present state. The previous state cannot jump to the next state without going through the present state.

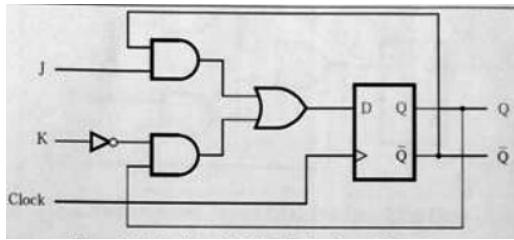II. ACTIVITY I

Write VHDL code to implement a JK flip-flop using a D flip-flop and the characteristic equation given. The D flip-flop needs to be implemented using a structural architecture style using the circuit shown in figure. The JK flip-flop must be constructed using a component declaration for a D flip-flop.



$$Q(t+1) = (J)(\overline{Q(t)}) + (\overline{K})(Q(t))$$

Fig. JK flip-flop using D flip-flop and characteristic equation

Write a VHDL test bench to verify the operation of the JK flip-flop and provide waveform.

VHDL Code

[comp1.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY comp1 IS PORT (
    i1, i2, a3, a4: IN STD_LOGIC;
    o1: OUT STD_LOGIC
);
END comp1;

ARCHITECTURE dataflow OF comp1 IS
BEGIN
    o1 <= ((i1 AND a4) or ((not i2) and
a3));
END dataflow;
```

[nand1.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND1 IS
    PORT(a , b: IN std_logic;
        o: OUT std_logic);
END NAND1;

ARCHITECTURE DATAFLOW OF NAND1 IS
BEGIN
    o <= a NAND b;
END DATAFLOW;
```

[nand2.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
```

```
ENTITY NAND_2 IS
    PORT(a, b, c: IN std_logic;
        o: OUT std_logic);
END NAND_2;

ARCHITECTURE DATAFLOW OF NAND_2 IS
BEGIN
    o <= NOT(a AND b AND c);
END DATAFLOW;
```

[dff.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY dff IS
    PORT( CLK , DATA: IN std_logic;
        Q, QBAR: OUT std_logic);
END dff;

ARCHITECTURE STRUC OF dff IS
    SIGNAL A, I1, I2, I3, I4: STD_LOGIC;
    SIGNAL I5: STD_LOGIC := '0';
    SIGNAL I6: STD_LOGIC := '1';

    COMPONENT NAND1
        PORT(a,b: IN std_logic;
            o : OUT std_logic
        );
    END COMPONENT;

    COMPONENT NAND_2
        PORT(a,b,c: IN std_logic;
            o : OUT std_logic
        );
    END COMPONENT;

    BEGIN
        Q <= I5;
        QBAR <= I6;
        O1: NAND1 PORT MAP (a => I2,
            b => I4, o=> I1);
        O2: NAND1 PORT MAP (a => CLK,
            b => I1, o=> I2);
        O4: NAND_2 PORT MAP (a => I2,
            b => CLK, c => I4, o=> I3);
        O3: NAND1 PORT MAP (a => I3,
            b => DATA, o=> I4);
        O5: NAND1 PORT MAP (a => I2,
            b => I6, o=> I5);
        O6: NAND1 PORT MAP (a => I5,
            b => I3, o=> I6);
    END STRUC;
```

[jkff.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY jkff IS
    PORT(CLOCK, J , K: IN std_logic;
```

```

        QT, QTBAR: INOUT std_logic);
END jkff;

ARCHITECTURE STRUC OF jkff IS
    SIGNAL A, A1: STD_LOGIC;
    SIGNAL A5: STD_LOGIC := '0';
    SIGNAL A6: STD_LOGIC := '1';

    COMPONENT dff
        PORT( CLK,DATA: IN std_logic;
              Q, QBAR : INOUT std_logic
            );
    END COMPONENT;

    COMPONENT comp1
        PORT(i1,i2,a3,a4:IN std_logic;
              o1: OUT std_logic
            );
    END COMPONENT;

    BEGIN
        QT <= A5;
        QTBAR <= A6;
        O1: comp1 PORT MAP(i1 => J, i2
=> K, a3 => A5, a4 => A6, o1 => A1);
        D1: dff PORT MAP(CLK => CLOCK,
DATA => A1, Q => A5, QBAR => A6);

    END STRUC;

```

Test bench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

ENTITY jkff_tb IS
END jkff_tb;

ARCHITECTURE behavioral OF jkff_tb IS
    COMPONENT jkff
        PORT (
            CLOCK: IN STD_LOGIC;
            J: IN STD_LOGIC;
            K: IN STD_LOGIC;
            QT: INOUT STD_LOGIC;
            QTBAR: INOUT STD_LOGIC
        );
    END COMPONENT;

    SIGNAL clock: STD_LOGIC;
    SIGNAL input_vector:
STD_LOGIC_VECTOR (1 DOWNTO 0) := "00";
    SIGNAL out1: STD_LOGIC:= '0';
    SIGNAL out2: STD_LOGIC:= '1';
    CONSTANT clk_p: time:= 10 ns;

    BEGIN
        uut: jkff PORT MAP(
            CLOCK => clock,

```

```

        J => input_vector(1),
        K => input_vector(0),
        QT => out1,
        QTBAR => out2
    );

    clkproc: PROCESS
    BEGIN
        clock <= '0';
        WAIT FOR clk_p/2;
        clock <= '1';
        WAIT FOR clk_p/2;
    END PROCESS clkproc;


    stim_proc: PROCESS
    BEGIN
        FOR index IN 0 TO 3 LOOP
            input_vector <=
std_logic_vector (to_unsigned(index,2));
            WAIT FOR 37 ns;
        END LOOP;
    END PROCESS;
END behavioral;

```

Discussion:


In this activity, we need to implement JK flip-flop using D flip-flop. Both JK and D flip-flop are implemented using component declaration. Separate components are made in separate files like nand1, nand2, comp1, dff and finally integrated in jkff. A test bench is written to verify the design of JK flip-flop.

Output:

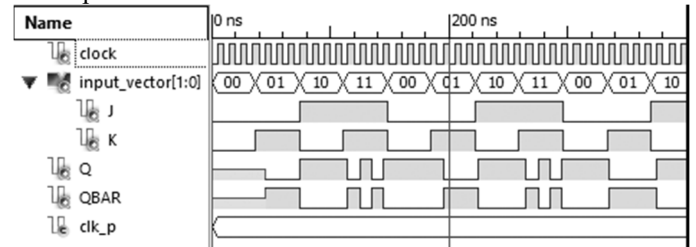

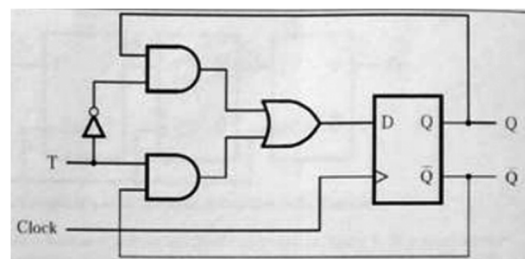III. ACTIVITY II

Write VHDL code to implement a T flip-flop using a D flip-flop and the characteristic equation given. The D flip-flop needs to be implemented using a structural architecture style using the circuit shown in figure. The T flip-flop must be constructed using a component declaration for a D flip-flop.



$$Q(t+1) = (T)(\overline{Q(t)}) + (\overline{T})(Q(t))$$

$$Q(t+1) = (T) \oplus (Q(t))$$

Fig. T flip-flop using D flip flop and its characteristic equation

Write a VHDL test bench to verify the operation of the T flip-flop and provide waveform

VHDL Code

[comp1.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY comp1 IS PORT (
    i1, i2, a3, a4: IN STD_LOGIC;
    o1: OUT STD_LOGIC
);
END comp1;

ARCHITECTURE dataflow OF comp1 IS
BEGIN
    o1 <= ((not i2 and a4) or (i1 and a3));
END dataflow;
```

[nand1.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND1 IS
    PORT(a , b: IN std_logic;
         o: OUT std_logic);
END NAND1;

ARCHITECTURE DATAFLOW OF NAND1 IS
BEGIN
    o <= a NAND b;
END DATAFLOW;
```

[nand2.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND_2 IS
    PORT(a, b, c: IN std_logic;
         o: OUT std_logic);
END NAND_2;

ARCHITECTURE DATAFLOW OF NAND_2 IS
BEGIN
    o <= NOT(a AND b AND c);
END DATAFLOW;
```

[dff.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY dff IS
```

```
    PORT( CLK , DATA: IN std_logic;
          Q, QBAR: OUT std_logic);
END dff;

ARCHITECTURE STRUC OF dff IS
    SIGNAL A, I1, I2, I3, I4: STD_LOGIC;
    SIGNAL I5: STD_LOGIC := '0';
    SIGNAL I6: STD_LOGIC := '1';

    COMPONENT NAND1
        PORT(a,b: IN std_logic;
             o : OUT std_logic
        );
    END COMPONENT;

    COMPONENT NAND_2
        PORT(a,b,c: IN std_logic;
             o : OUT std_logic
        );
    END COMPONENT;

    BEGIN
        Q <= I5;
        QBAR <= I6;
        O1: NAND1 PORT MAP (a => I2,
                             b => I4, o=> I1);
        O2: NAND1 PORT MAP (a => CLK,
                             b => I1, o=> I2);
        O4: NAND_2 PORT MAP (a => I2,
                             b => CLK, c => I4, o=> I3);
        O3: NAND1 PORT MAP (a => I3,
                             b => DATA, o=> I4);
        O5: NAND1 PORT MAP (a => I2,
                             b => I6, o=> I5);
        O6: NAND1 PORT MAP (a => I5,
                             b => I3, o=> I6);
    END STRUC;

[hff.vhd]
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY tff IS
    PORT( CLOCK, T, TNOT: IN STD_LOGIC;
          QT, QTBAR: INOUT STD_LOGIC);
END tff;

ARCHITECTURE STRUC OF tff IS
    SIGNAL A, A1: STD_LOGIC;
    SIGNAL A5: STD_LOGIC := '0';
    SIGNAL A6: STD_LOGIC := '1';

    COMPONENT dff
        PORT( CLK, DATA: IN STD_LOGIC;
              Q, QBAR : INOUT STD_LOGIC
        );
    END COMPONENT;

    COMPONENT comp1
```

```

        PORT(i1,i2,a3,a4:IN STD_LOGIC;
              o1: OUT STD_LOGIC
        );
    END COMPONENT;

    BEGIN
        QT <= A5;
        QTBAR <= A6;
        O1: comp1 PORT MAP(i1 => T, i2
=> TNOT, a3 => A6, a4 => A5, o1 => A1);
        D1: dff PORT MAP(CLK => CLOCK,
DATA => A1, Q => A5, QBAR => A6);

    END STRUC;

```

Test Bench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

ENTITY tff_tb IS
END tff_tb;

ARCHITECTURE behavioral OF tff_tb IS
    COMPONENT tff
    PORT (
        CLOCK: IN STD_LOGIC;
        T: IN STD_LOGIC;
        TNOT: IN STD_LOGIC;
        QT: INOUT STD_LOGIC;
        QTBAR: INOUT STD_LOGIC
    );
    END COMPONENT;

    SIGNAL clk: STD_LOGIC;
    SIGNAL input, ninput: STD_LOGIC;
    SIGNAL out1: STD_LOGIC:= '1';
    SIGNAL out2: STD_LOGIC:= '1';
    CONSTANT clk_p: time:= 10 ns;

    BEGIN
        uut: tff PORT MAP(
            CLOCK => clk,
            T => input,
            TNOT => ninput,
            QT => out1,
            QTBAR => out2
        );

        clkproc: PROCESS
        BEGIN
            clk <= '0';
            WAIT FOR clk_p/2;
            clk <= '1';
            WAIT FOR clk_p/2;
        END PROCESS clkproc;

        stim_proc: PROCESS
        BEGIN

```

```

            if out1 = 'U' then
                input <= '0';
                ninput <= '0';
                WAIT FOR 37 ns;
            end if;

            input <= '1';
            ninput <= not input;
            WAIT FOR 37 ns;


        END PROCESS stim_proc;
    END behavioral;

```

Discussion:

As in first activity, D flip-flop is to be implemented as component for designing T flip-flop. So, component required for D flip-flop is same as in previous activity. Only small portion of code in JK flip-flop is changed for T flip-flop as T flip-flop has only one input and behaves same as JK flip-flop while giving same value in J and K. A test bench is written to verify the operation of T flip-flop.

Output:

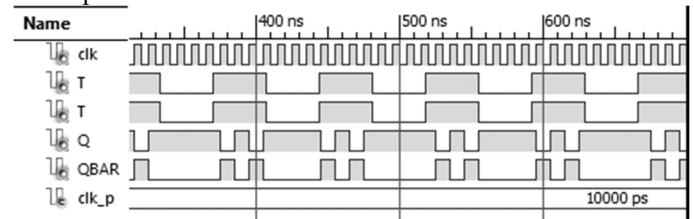

IV. ACTIVITY III

Use VHDL to implement a 4-bit serial in serial out (SISO) right-shift register. Determine the output of the shift register after the input sequence 01010101 has been shifted eight times starting with the most significant bit. Assume that the output of the shift register is reset initially to 0000. The shift-register must be constructed with D flip-flops using a component declaration for a D flip-flop.

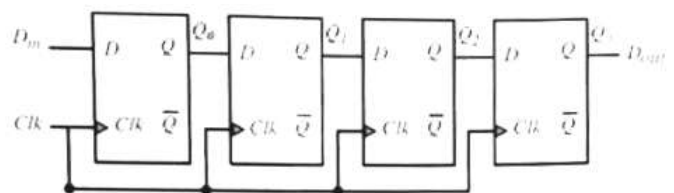


Fig. SISO right shift register using D flip-flop

Write a VHDL test bench to verify the operation of the 4-bit SISO and provide appropriate waveforms.

VHDL Code

[nand1.vhd]

```

LIBRARY IEEE;

```

```

USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND1 IS
    PORT(a , b: IN std_logic;
          o: OUT std_logic);
END NAND1;

ARCHITECTURE DATAFLOW OF NAND1 IS
BEGIN
    o <= a NAND b;
END DATAFLOW;

[nand2.vhd]
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY NAND_2 IS
    PORT(a, b, c: IN std_logic;
          o: OUT std_logic);
END NAND_2;

ARCHITECTURE DATAFLOW OF NAND_2 IS
BEGIN
    o <= NOT(a AND b AND c);
END DATAFLOW;

[dff.vhd]
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY dff IS
    PORT( CLK , DATA: IN std_logic;
          Q, QBAR: OUT std_logic);
END dff;

ARCHITECTURE STRUC OF dff IS
    SIGNAL A, I1, I2, I3, I4: STD_LOGIC;
    SIGNAL I5: STD_LOGIC := '0';
    SIGNAL I6: STD_LOGIC := '1';

    COMPONENT NAND1
        PORT( a,b: IN std_logic;
              o : OUT std_logic
        );
    END COMPONENT;

    COMPONENT NAND_2
        PORT( a,b,c: IN std_logic;
              o : OUT std_logic
        );
    END COMPONENT;

BEGIN
    Q <= I5;
    QBAR <= I6;
    O1: NAND1 PORT MAP (a => I2,
                        b => I4, o=> I1);
    O2: NAND1 PORT MAP (a => CLK,
                        b => I1, o=> I2);

```

```

O4: NAND_2 PORT MAP (a => I2,
                    b => CLK, c => I4, o=> I3)
O3: NAND1 PORT MAP (a => I3,
                    b => DATA, o=> I4);
O5: NAND1 PORT MAP (a => I2,
                    b => I6, o=> I5);
O6: NAND1 PORT MAP (a => I5,
                    b => I3, o=> I6);

END STRUC;

```

[siso.vhd]

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY siso IS
    PORT( CLOCK, Din: IN STD_LOGIC;
          QA, QB, QC: INOUT STD_LOGIC;
          Dout, QTBAR: INOUT STD_LOGIC);
END siso;

ARCHITECTURE STRUC OF siso IS
    SIGNAL Q0, Q0B, Q1, Q1B, Q2, Q2B, Q3,
    Q3B, A1: STD_LOGIC;
    SIGNAL A5: STD_LOGIC := '0';
    SIGNAL A6: STD_LOGIC := '1';

    COMPONENT dff
        PORT( CLK, DATA: IN STD_LOGIC;
              Q, QBAR : INOUT STD_LOGIC
        );
    END COMPONENT;

    COMPONENT comp1
        PORT(i1,i2,a3,a4:IN STD_LOGIC;
              o1: OUT STD_LOGIC
        );
    END COMPONENT;

BEGIN
    Dout <= A5;
    QTBAR <= A6;
    QA <= Q0;
    QB <= Q1;
    QC <= Q2;
    D1: dff PORT MAP (CLK => CLOCK,
    DATA => Din, Q => Q0, QBAR => Q0B);
    D2: dff PORT MAP (CLK => CLOCK,
    DATA => Q0, Q => Q1, QBAR => Q1B);
    D3: dff PORT MAP (CLK => CLOCK,
    DATA => Q1, Q => Q2, QBAR => Q2B);
    D4: dff PORT MAP (CLK => CLOCK,
    DATA => Q2, Q => A5, QBAR => A6);

END STRUC;

```

Test Bench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

```

```

ENTITY siso_tb IS
END siso_tb;

ARCHITECTURE behavioral OF siso_tb IS
    COMPONENT siso
    PORT (
        CLOCK: IN STD_LOGIC;
        Din: IN STD_LOGIC;
        QA, QB, QC: INOUT STD_LOGIC;
        Dout: INOUT STD_LOGIC;
        QTBAR: INOUT STD_LOGIC
    );
END COMPONENT;

    SIGNAL clk: STD_LOGIC;
    SIGNAL input: STD_LOGIC;
    signal input_seq: STD_LOGIC_VECTOR(7
downto 0):= "10101010";
    SIGNAL qa, qb, qc: std_logic;
    SIGNAL out1: STD_LOGIC:= '1';
    CONSTANT clk_p: time:= 10 ns;

BEGIN
    uut: siso PORT MAP(
        CLOCK => clk,
        QA => qa,
        QB => qb,
        QC => qc,
        Din => input,
        Dout => out1
    );

    clkproc: PROCESS
    BEGIN
        clk <= '0';
        WAIT FOR clk_p/2;
        clk <= '1';
        WAIT FOR clk_p/2;
    END PROCESS clkproc;

    stim_proc: PROCESS
    BEGIN
        for index in 1 to 8 loop
            input <= input_seq(7);
            input_seq(7 downto 1) <=
            input_seq(6 downto 0);
            input_seq(0) <= '0';
            WAIT FOR 15 ns;
        end loop;
        wait;
    END PROCESS stim_proc;


END behavioral;

```

Discussion:

This is another example of using D flip-flop as component. Here D flip-flop is implemented to design shift register. Four D flip-flop is required to design four bit serial in serial out right

 shift register. D flip-flop code in vhdl is borrowed from previous activity and structural declaration of shift register is made using D flip-flop as its major component. A test bench was made and checked for input sequence of '10101010' whose output is given below.



V. ACTIVITY IV

Use VHDL to implement a 4-bit synchronous up counter. In a synchronous counter all flip-flop receive a common clock signal and change their states at the same time. The shift-register must be constructed with T flip-flops using a component declaration for a T flip-flop.

 


Fig. Synchronous up counter using T flip-flop

Write a VHDL test bench to verify the operation of the 4-bit synchronous up counter and provide appropriate waveforms.

VHDL Code

[tff.vhd]

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY tff IS
    PORT(CLOCK, RESET, T: IN STD_LOGIC;
        QT: OUT STD_LOGIC);
END tff;

ARCHITECTURE behav OF tff IS
    SIGNAL output: STD_LOGIC;

    BEGIN
        PROCESS(RESET, CLOCK)
        BEGIN
            IF RESET = '1' THEN
                output <= '0';
            ELSIF CLOCK'EVENT AND
            CLOCK='1' THEN

```

```

        IF T = '0' THEN
            output <= output;
        ELSIF T = '1' THEN
            output <= NOT output;
        ELSE output <= 'U';
        END IF;
    END IF;
END PROCESS;
QT <= output;

END BEHAV;

[syncup.vhd]
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY syncup IS
    PORT(clock,reset,input:IN STD_LOGIC;
        data: out std_logic_vector(3
downto 0) );
END syncup;

architecture struc of syncup is
    COMPONENT tff
        PORT( CLOCK, RESET, T: IN
STD_LOGIC;
            QT: OUT STD_LOGIC
        );
    END COMPONENT;

    signal temp: std_logic_vector(3
downto 0) := "0000";
    signal and_1, and_2: std_logic;
    begin
        and_1 <= temp(0) and temp(1);
        and_2 <= temp(2) and and_1;

        d0 : tff port map (CLOCK =>
clock, RESET => reset, T => '1', QT =>
temp(0));

        d1 : tff port map (CLOCK =>
clock, RESET => reset, T => temp(0), QT
=> temp(1));

        d2 : tff port map (CLOCK =>
clock, RESET => reset, T => and_1, QT =>
temp(2));

        d3 : tff port map (CLOCK =>
clock, RESET => reset, T => and_2, QT =>
temp(3));

        data <= temp;

end struc;

```

Test Bench

```
LIBRARY ieee;
```

```

USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY syncup_tb IS
END syncup_tb;

ARCHITECTURE behavior OF syncup_tb IS
    COMPONENT syncup
        PORT(
            clock: IN std_logic;
            input: IN std_logic;
            reset: IN std_logic;
            data: out std_logic_vector(3
downto 0) );
    END COMPONENT;

    SIGNAL clock: std_logic := '0';
    SIGNAL reset: std_logic := '1';
    SIGNAL input: std_logic := '1';
    SIGNAL data: std_logic_vector(3
downto 0);

    BEGIN
        uut: syncup PORT MAP(
            clock => clock,
            input => input,
            reset => reset,
            data => data
        );

        clk: PROCESS
        BEGIN
            wait for 5ns;
            clock <= not clock;
        END PROCESS clk;

        main: PROCESS
        BEGIN
            wait for 7 ns;
            reset <= '0';

            wait for 20ns;
            input <= '1';

            wait;
        END PROCESS main;


    END behavior;

```

Discussion:

Synchronous up counter is made using component declaration for T flip-flop. For simplicity T flip-flop is made in behavioural model. While declaring component for synchronous counter, block diagram given with the question provided great help in proper connection of components. A test bench is written to verify the operation of this activity.

Output :

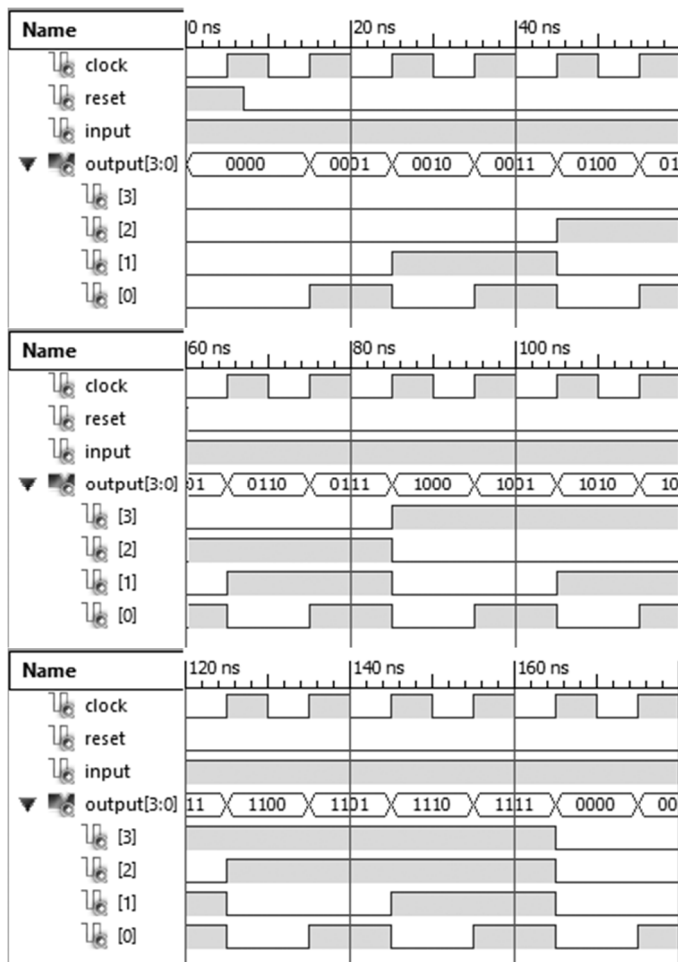

VI. ACTIVITY V

Use VHDL to design an asynchronous decade counter. The 10 states of a decade counter represent the BCD numbers from 0 to 9. In asynchronous counters, only the first flip-flop is clocked by an external clock signal, and each successive flip-flop is clocked by the output of the preceding flip-flop. Asynchronous counters are also referred to as ripple counters because the information ripples from the less significant bit to the more significant bit, one bit at a time. The asynchronous decade counter must be constructed with T flip-flops using a component declaration for a T flip-flop.

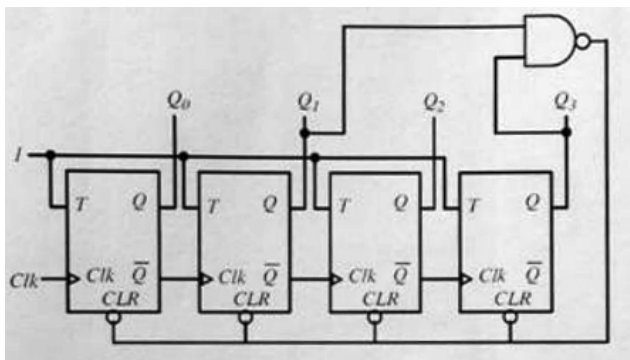


Fig. Asynchronous Decade Counter

Write a VHDL test bench to verify the operation of the decade counter and provide appropriate waveforms.

VHDL Code

[tff.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY tff IS
    PORT(CLOCK, RESET, T: IN STD_LOGIC;
          QT: OUT STD_LOGIC);
END tff;

ARCHITECTURE behav OF tff IS
    SIGNAL output: STD_LOGIC;

    BEGIN
        PROCESS(RESET, CLOCK)
        BEGIN
            IF RESET = '1' THEN
                output <= '0';
            ELSIF CLOCK'EVENT AND
CLOCK='1' THEN
                IF T = '0' THEN
                    output <= output;
                ELSIF T = '1' THEN
                    output <= NOT output;
                ELSE output <= 'U';
                END IF;
            END IF;
        END PROCESS;
        QT <= output;
    END BEHAV;
```

[asynccdec.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY asynccdec IS
    PORT( clock, input: IN STD_LOGIC;
          data : out std_logic_vector(3
downto 0) );
END asynccdec;

architecture struc of asynccdec is
    COMPONENT tff
        PORT( CLOCK, RESET, T: IN
STD_LOGIC;
              QT, QTBAR: OUT STD_LOGIC
        );
    END COMPONENT;

    signal temp : std_logic_vector(3
downto 0) := "0000";
    signal ntemp : std_logic_vector(3
downto 0) := "1111";
    signal and_1 : std_logic := '1';
```

```

begin
    and_1 <= temp(1) and temp(3);
    d0 : tff port map (CLOCK =>
clock, RESET => and_1, T => input, QT =>
temp(0), QTBAR => ntemp(0));

    d1 : tff port map (CLOCK =>
ntemp(0), RESET => and_1, T => input, QT
=> temp(1), QTBAR => ntemp(1));

    d2 : tff port map (CLOCK =>
ntemp(1), RESET => and_1, T => input, QT
=> temp(2), QTBAR => ntemp(2));

    d3 : tff port map (CLOCK =>
ntemp(2), RESET => and_1, T => input, QT
=> temp(3), QTBAR => ntemp(3));

    data <= temp;

end struc;

```

(a) Test Bench

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;

ENTITY asyncdec_tb IS
END asyncdec_tb;
ARCHITECTURE behavior OF asyncdec_tb IS
    COMPONENT asyncdec
        PORT( clock : IN std_logic;
              input : IN std_logic;
              data : std_logic_vector(3
downto 0) : out
END COMPONENT;

    SIGNAL clock : std_logic := '1';
    SIGNAL input : std_logic;
    SIGNAL data : std_logic_vector(3
downto 0) := "0000";

    BEGIN
        uut: asyncdec PORT MAP(
            clock => clock,
            input => input,
            data => data
        );

        clk: PROCESS
        BEGIN
            wait for 5ns;
            clock <= not clock;
        END PROCESS clk;

        main: PROCESS
        BEGIN
            input <= '1';

```

```


        wait;
    END PROCESS main;

END behavior;

```

Discussion:

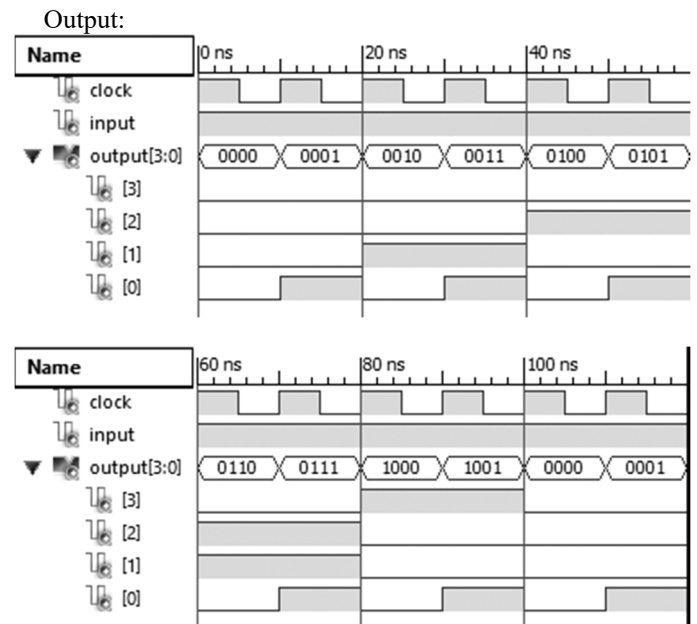Asynchronous counter are those in which all flip-flops do not receive same clock pulse. Rather output from preceding flip-flop act as clock for next flip-flop. In this activity, we implemented T flip-flop as main component and designed an asynchronous decade counter. The operation of this counter was verified using a test bench simulation. Output waveform is shown below.



VII. ACTIVITY VI

Use VHDL to design a four bit Johnson counter. A Johnson counter generates a sequence of the binary numbers where only one bit position changes between two consecutive numbers. Starting with an initial value of Q0Q1Q2Q3 equal to 0000, the Johnson counter periodically generates the sequence 0000, 1000, 1100, 1110, 1111, 0111, 0011, 0001, and 0000. Notice that only one bit position changes between two consecutive numbers, as in the case of the Gray code. For a Johnson counter to work properly, it must be reset initially to 0000. The Johnson counter must be constructed using a component declaration for a D flip-flops.

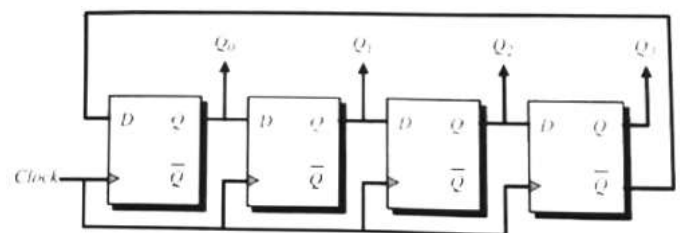


Fig. Johnson Counter

Write a VHDL test bench to verify the operation of the Johnson counter and provide appropriate waveforms.

VHDL Code:

[dff.vhd]

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

ENTITY dff IS
    PORT( CLK , DATA: IN std_logic;
          Q, QBAR: OUT std_logic);
END dff;

ARCHITECTURE STRUC OF dff IS
    BEGIN
        PROCESS (CLK, DATA)
        BEGIN
            IF (CLK'EVENT AND CLK = '1')
            THEN Q <= DATA;
                QBAR <= NOT DATA;
            END IF;
        END PROCESS;
    END STRUC;
```

[johnson.vhd]

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity johnson is Port (
    clock : in std_logic;
    reset : in std_logic;
    data : out std_logic_vector(3 downto
0) );
end johnson;

architecture struc of johnson is
    COMPONENT dff
        PORT( clock : in std_logic;
              reset : in std_logic;
              d : in std_logic;
              q : out std_logic
        );
    END COMPONENT;

    signal temp : std_logic_vector(3
downto 0) := "0000";
    signal wir : std_logic := '0';
    begin
        wir <= not temp(0);
        d0 : dff port map (reset =>
reset, clock => clock, d => wir, q =>
temp(3));
```

```
        d1 : dff port map (reset =>
reset, clock => clock, d => temp(3), q =>
temp(2));
```

```
        d2 : dff port map (reset =>
reset, clock => clock, d => temp(2), q =>
temp(1));
```

```
        d3 : dff port map (reset =>
reset, clock => clock, d => temp(1), q =>
temp(0));
```

```
        data <= temp;
```

```
    end struc;
```

Test Bench

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY johnson_tb IS
END johnson_tb;

ARCHITECTURE behavior OF johnson_tb IS
    COMPONENT johnson
        PORT( clock : IN std_logic;
              reset : IN std_logic;
              data : out
std_logic_vector(3 downto 0) );
    END COMPONENT;

    SIGNAL clock : std_logic := '0';
    SIGNAL reset : std_logic := '1';
    SIGNAL data : std_logic_vector(3
downto 0);

    BEGIN
        uut: johnson PORT MAP(
            clock => clock,
            reset => reset,
            data => data
        );

        clk: PROCESS
        BEGIN
            wait for 5ns;
            clock <= not clock;
        END PROCESS clk;

        main: PROCESS
        BEGIN
            reset <= '1';
            wait for 20ns;


            reset <= not reset;
            wait;
        END PROCESS main;

    END behavior;
```

Discussion:

Johnson counter is also called ring counter in which there is change in only one bit in one clock pulse. In above VHDL code, Johnson counter is made using component declaration for D flip-flop as instructed. A test bench is used for output waveform which is shown below.

Output:

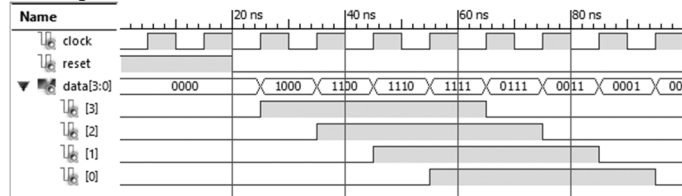

VIII. ACTIVITY VII

Use VHDL to create a 2-bit BCD counter as shown. The BCD counter consists of two 1 bit BCD counters cascaded to form a 2-bit BCD counter. The 2-bit BCD counter counts from 00 to 99. Notice that both 1-bit BCD counters are initialized by a load data input of 0. The 2-bit BCD counter must be constructed using component declarations for the D flip-flops.

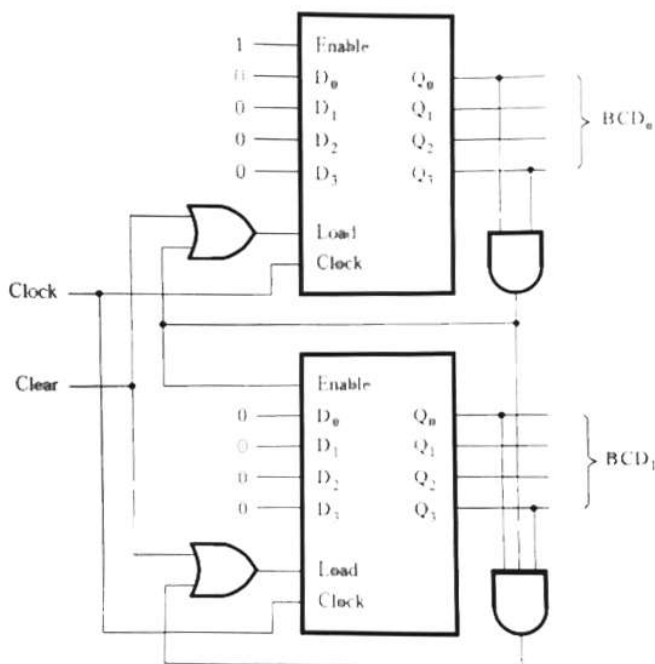


Fig. Block diagram for 2-bit BCD counter

VHDL Code:

[dff.vhd]

```
library ieee;
use IEEE.STD_LOGIC_1164.ALL;

entity dff is
    port (
        d      : in STD_LOGIC;
        clock  : in STD_LOGIC;
        reset  : in STD_LOGIC;
        q      : out STD_LOGIC
    );
```

```
);
end dff;

architecture behave of dff is
begin
    process(reset, clock)
    begin
        if (reset = '1')
            then q <= '0';
        elsif (clock'event and clock =
'1') then
            q <= d;
        end if;
    end process;
end behave;
```

[bcd1.vhd]

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity bcd is Port (
    clock : in std_logic;
    load : in std_logic;
    enable : in std_logic;
    reset : in std_logic;
    data : in std_logic_vector (3 downto
0);
    output : out std_logic_vector (3
downto 0) );
end bcd;

architecture struc of bcd is
    COMPONENT dff
        PORT(
            clock : in std_logic;
            reset : in std_logic;
            d      : in std_logic;
            q      : out std_logic
        );
    END COMPONENT;

    signal temp : std_logic_vector(3
downto 0) := "0000";
```

```
begin
    d0 : dff port map (reset =>
reset, clock => clock, d => data(3), q =>
temp(3));

    d1 : dff port map (reset =>
reset, clock => clock, d => data(2), q =>
temp(2));

    d2 : dff port map (reset =>
reset, clock => clock, d => data(1), q =>
temp(1));
```

```

        d3 : dff port map (reset =>
reset, clock => clock, d => data(0), q =>
temp(0));

```

```

        output <= temp;

```

```

end struc;

```

Test bench

```

LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;
USE IEEE.NUMERIC_STD.ALL;

```

```

ENTITY bcd_tb IS
END bcd_tb;

```

```

ARCHITECTURE behavioral OF bcd_tb IS
    COMPONENT bcd
    PORT (
        reset: IN STD_LOGIC;
        clock: IN STD_LOGIC;
        load: IN STD_LOGIC;
        enable: IN STD_LOGIC;
        data: IN STD_LOGIC_VECTOR(3
DOWNT0 0);
        output: out STD_LOGIC_VECTOR(3
DOWNT0 0)
    );
    END COMPONENT;

```

```

    SIGNAL clock: STD_LOGIC;
    SIGNAL load: STD_LOGIC;
    SIGNAL enable: STD_LOGIC;
    SIGNAL out1: STD_LOGIC_VECTOR(3
DOWNT0 0):= "0000";
    SIGNAL data: STD_LOGIC_VECTOR(3
DOWNT0 0):= "0000";
    SIGNAL reset: STD_LOGIC:= '1';

```

```

    CONSTANT clk_p: time:= 10 ns;

```

```

BEGIN

```

```

    uut: bcd PORT MAP(
        clock => clock,
        load => load,
        reset => reset,
        enable => enable,
        data => data,
        output => out1
    );

```

```

    clkproc: PROCESS
    BEGIN
        clock <= '0';
        WAIT FOR clk_p/2;

```

```

        clock <= '1';
        WAIT FOR clk_p/2;
    end process clkproc;

```

```

    stim_proc: PROCESS

```

```

    BEGIN

```

```

        wait for 5 ns;
        reset <= '0';
        enable <= '1';
        data <= "0000";
        wait;

```

```

    END PROCESS;

```

```




END behavioral;








```

Discussion:

In this activity, we need to make 2 bit bcd counter using D flip-flop. This can be done using two one bit decade counter that can count from 0 to 9. For each cycle in least significant bit, one clock pulse is send to most significant bit. Hence clock of second 1 bit counter is connected to condition of trigger next bit in first 1 bit counter. VHDL code along with test bench is given above. BCD counter is implemented using D flip-flop which is defined in behavioural model for simplicity.

Output:

  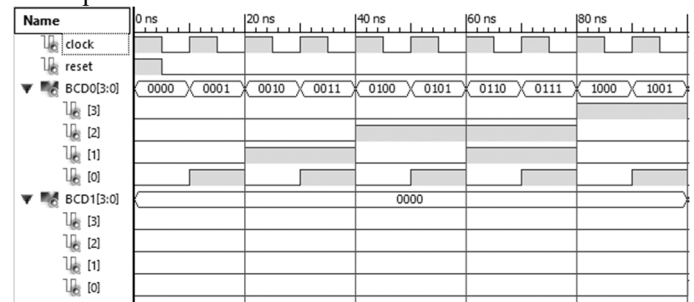

       

APPENDIX

Appendix A

Logic circuit for positive edge triggered D flip-flop

 


Figure showing positive edge triggered logic circuit using NAND Gate. This diagram is followed to implement D flip-flop in structural model

CONCLUSION

Various activities concerned with sequential logic design using VHDL programming were done. Different logic circuits were designed mostly using flip-flops mostly using structural model where components are defined in behavioral model for simplicity. Test bench for each activity is made to generate output waveforms. Simulation was done in Xilinx ISE Design Suite. VHDL codes and waveform to all activities are included in this report.

ACKNOWLEDGMENT

This lab report is prepared as a document for activities done that is concerned with sequential logic design using VHDL programming. This report is made accurate and professional as far as possible. I would like to express our deepest gratitude to our teacher, Mr. Dinesh Baniya Kshatri, for guiding us in the practical. I am very grateful to the Department of Electronics and Computer Engineering (DoECE) of IOE Central Campus, Pulchowk for arranging such a schedule on our academic side.

REFERENCES

- [1] (2016) The Wikipedia website. [Online]. Available: <https://en.m.wikipedia.org/wiki/VHDL/>
- [2] P. J. Ashenden, The VHDL Cookbook [portable document]. Available: <http://www.cs.adelaide.edu.au/>
- [3] (2016) The edaboard website. [Online]. Available: <http://www.edaboard.com/thread/77216.html/>
- [4] (2016) The Stack Overflow website. [Online]. Available: <http://www.stackflow.com/>
- [5] (2016) The asic-world website. [Online]. Available: http://www.asic-world.com/examples/vhdl/t_ff.html/
- [6] (2016) The ohio.edu website. [Online]. Available: <http://www.ohio.edu/people/starzykj/webcad/EE4143/packages.html/>
- [7] (2016) DFF Test bench [Online]. Available: http://esd.cs.ucr.edu/labs/tutorial/tb_dff.vhd/
- [8] (2016) The Wikibooks website. [Online]. Available: http://en.m.wikibooks/wiki/VHDL_for_FPGA_Design/T_Flip_Flop/
- [9] S. Brown and Z. Vranesic, "Flip-flops, registers, counters and a simple processor" in Fundamental of *Digital Logic with VHDL Design*, 2nd ed., the United States: McGraw-Hill, 2005.
- [10] D. Kshatri, Sequential Logic Design using VHDL [scanned document]. Available: Offline.
- [11] S. Shrestha, VHDL [presentation]. Available: Offline